

Day 4, Session 2: Advanced FSMs - Pattern Detection & Mealy Machines

Concept Block (12 min)

Sequence Detector - The Classic FSM Problem

Problem: Design a circuit that detects the pattern "1011" in a serial input stream.

Example input stream:

Input: 0 1 0 1 1 0 1 0 1 1 1 0 1 1 ...
 — — — —————| — —————|
 Pattern! Pattern!
Output: 0 0 0 0 0 0 0 1 0 0 0 0 0 1 ...
 ↑ ↑
 Detected! Detected!

This is used in:

- Frame synchronization (networking)
- Start-of-packet detection (UART, USB)
- Pattern recognition (bioinformatics, signal processing)
- Error detection codes

Two Approaches: Overlapping vs Non-Overlapping

Non-Overlapping Detection:

Patterns **cannot share bits**.

Input: 1 0 1 1 0 1 1 ...
 —————| —————|
 Pattern 1 Pattern 2

After detecting "1011", restart from scratch.

Overlapping Detection:

Patterns **can share bits**.

Input: 1 0 1 1 1 ...
 —————|
 Pattern 1
 —————|
 Pattern 2 (shares the "1011" with pattern 1)

After detecting "1011", check if the last bits can start a new pattern.

We'll implement overlapping detection (more complex, more useful).

State Diagram Design Process

Step-by-step design for "1011" detector:

States needed:


1. **IDLE**: No pattern progress (or just saw 0)
2. **S1**: Saw "1"
3. **S10**: Saw "10"
4. **S101**: Saw "101"
5. **S1011**: Saw "1011" - **DETECTED!** (but immediately check if we can continue)


Actually, we can optimize to 4 states:

1. **S0**: Idle / No progress
2. **S1**: Saw "1"
3. **S10**: Saw "10"
4. **S101**: Saw "101"

When we see the 4th bit (1), we detect the pattern and can transition directly.

State Diagram: Sequence Detector (Mealy)

 

 

Key Mealy Feature: Output=1 happens **on the transition**, not in a state!

Mealy vs Moore for Sequence Detection

Mealy Approach (What we'll build):

```
// Output depends on current_state AND input
if (current_state == S101 && in == 1)
    detected = 1; // Output immediately
```

Advantages:

- Fewer states needed
- Faster response (output on same cycle as detection)
- More compact

Disadvantages:

- Output can glitch if input changes
- Harder to verify

Moore Approach (Alternative):

```
// Need an extra "DETECTED" state
// Output depends only on state
```

```
States: S0, S1, S10, S101, S1011_DETECTED
// Output=1 only in S1011_DETECTED state
```

Advantages:

- Glitch-free outputs
- Easier to verify
- More intuitive

Disadvantages:

- Requires extra state
- 1 clock cycle delay in output

Code & Practical Block (15 min)

Implementation: Sequence Detector (Mealy Machine)

// sequence_detector.v - Detects "1011" pattern (Mealy FSM)

```
module sequence_detector (
    input  wire clk,
    input  wire rst,
    input  wire in,          // Serial input stream
    output reg  detected     // 1 when "1011" detected
);
```

// State encoding

localparam S0 = 2'b00; // Idle / No progress

localparam S1 = 2'b01; // Saw "1"

localparam S10 = 2'b10; // Saw "10"

localparam S101 = 2'b11; // Saw "101"

// State registers

reg [1:0] current_state;

reg [1:0] next_state;

// Block 1: State Register (Sequential)

always @(posedge clk or posedge rst) begin

if (rst)

current_state <= S0;

else

current_state <= next_state;

end

// Block 2: Next State Logic (Combinational)

```

always @(*) begin
    case (current_state)
        S0: begin
            if (in)
                next_state = S1;    // Saw first "1"
            else
                next_state = S0;    // Stay in idle
            end

        S1: begin
            if (in)
                next_state = S1;    // Another "1", restart pattern
            else
                next_state = S10;   // Saw "10"
            end

        S10: begin
            if (in)
                next_state = S101;  // Saw "101"
            else
                next_state = S0;     // Broke pattern, restart
            end

        S101: begin
            if (in)
                next_state = S10;   // Saw "1011"! Overlap: "10" of next
pattern
            else
                next_state = S10;   // Saw "1010", continue with "10"
            end

        default: next_state = S0;
    endcase
end

// Block 3: Output Logic (Combinational - MEALY)
always @(*) begin

```

```

        // Mealy: Output depends on current_state AND input
        if (current_state == S101 && in == 1)
            detected = 1;          // Pattern "1011" detected!
        else
            detected = 0;
        end

endmodule

```

Line-by-Line: Key Differences from Moore

Output Logic (Mealy - Lines 62-68):

```

always @(*) begin
    if (current_state == S101 && in == 1) // ← Depends on INPUT!
        detected = 1;
    else
        detected = 0;
    end
end

```

Critical difference from Moore:

- **Moore:** if (current_state == DETECTED_STATE)
- **Mealy:** if (current_state == S101 && in == 1)

Mealy output changes IMMEDIATELY when input changes (combinational path from input to output).

Overlapping Detection (Lines 50-53):

```

S101: begin
    if (in)
        next_state = S10;    // Detected "1011", but "10" starts next pattern!
    else
        next_state = S10;    // Saw "1010", have "10" for next attempt
    end
end

```

Why transition to S10?


Input stream: ...1 0 1 1 1...

—————| Pattern detected!

———| These bits ("10") start checking for next pattern

Without overlap, we'd go back to S0 and miss patterns like:

Input: 1 0 1 1 0 1 1

 

Testbench: Sequence Detector

```
// tb_sequence_detector.v
module tb_sequence_detector;

    reg  clk, rst, in;
    wire detected;

    sequence_detector uut (
        .clk(clk),
        .rst(rst),
        .in(in),
        .detected(detected)
    );

    // Clock generator
    initial begin
        clk = 0;
        forever #5 clk = ~clk;
    end

    // Test stimulus
    initial begin
        $dumpfile("sequence_detector.vcd");
        $dumpvars(0, tb_sequence_detector);

        $display("Time | in | detected | State | Pattern Progress");
        $display("-----");

        // Initialize
        rst = 1; in = 0;
        #10;
        rst = 0;
        #10;
```

```

// Test sequence: 0 1 0 1 1 0 1 0 1 1 1
//               _____|
//               Pattern!   Overlapping pattern!

$display("\n--- Input: 0 (idle) ---");
in = 0; #10;

$display("\n--- Input: 1 (start pattern) ---");
in = 1; #10;

$display("\n--- Input: 0 (now have '10') ---");
in = 0; #10;

$display("\n--- Input: 1 (now have '101') ---");
in = 1; #10;

$display("\n--- Input: 1 (DETECT '1011'!) ---");
in = 1; #10;

$display("\n--- Input: 0 (break pattern) ---");
in = 0; #10;

$display("\n--- Input: 1 (restart) ---");
in = 1; #10;

$display("\n--- Input: 0 (have '10') ---");
in = 0; #10;

$display("\n--- Input: 1 (have '101') ---");
in = 1; #10;

$display("\n--- Input: 1 (DETECT '1011' again!) ---");
in = 1; #10;

$display("\n--- Input: 1 (have '101' from overlap) ---");

```



```

        in = 1; #10;

        $display("\n--- Input: 1 (DETECT '1011' third time!) ---");
        // Current state is S10 (from "11"), next "1" gives S101, then "1"
detects!
        in = 1; #10;

        #20;
        $finish;
end

// Monitor state changes
always @(posedge clk) begin
    $display("%4t | %b | %b | %s | %s",
            $time, in, detected,
            (uut.current_state == 2'b00) ? "S0 " :
            (uut.current_state == 2'b01) ? "S1 " :
            (uut.current_state == 2'b10) ? "S10 " :
            (uut.current_state == 2'b11) ? "S101" : "??? ",
            (uut.current_state == 2'b00) ? "Idle" :
            (uut.current_state == 2'b01) ? "Saw: 1" :
            (uut.current_state == 2'b10) ? "Saw: 10" :
            (uut.current_state == 2'b11) ? "Saw: 101" : "Unknown");
end

endmodule

```

Expected Behavior

Time | in | detected | State | Pattern Progress

--- Input: 0 (idle) ---

25		0		0		S0		Idle
----	--	---	--	---	--	----	--	------

--- Input: 1 (start pattern) ---

35		1		0		S1		Saw: 1
----	--	---	--	---	--	----	--	--------

```

--- Input: 0 (now have '10') ---
45 | 0 | 0 | S10 | Saw: 10

--- Input: 1 (now have '101') ---
55 | 1 | 0 | S101 | Saw: 101

--- Input: 1 (DETECT '1011'!) ---
65 | 1 | 1 | S10 | DETECTED!  (now have '10' for overlap)

--- Input: 0 (break pattern) ---
75 | 0 | 0 | S0 | Idle

--- Input: 1 (restart) ---
85 | 1 | 0 | S1 | Saw: 1

--- Input: 0 (have '10') ---
95 | 0 | 0 | S10 | Saw: 10

--- Input: 1 (have '101') ---
105 | 1 | 0 | S101 | Saw: 101

--- Input: 1 (DETECT '1011' again!) ---
115 | 1 | 1 | S10 | DETECTED! 

```

Compile and Test

```

iverilog -o sim/seq_det sequence_detector.v tb_sequence_detector.v
vvp sim/seq_det
gtkwave sequence_detector.vcd

```

Mini Task (10 min)

Build a "101" sequence detector (simpler pattern):

Requirements:

1. Detect pattern "101"
2. Use Mealy machine (output on transition)
3. Support overlapping detection
4. Use 3-block coding style

States needed:

- S0: Idle
- S1: Saw "1"
- S10: Saw "10"
- (No S101 state - detect on transition!)

Template:

```
module seq_101_detector (  
    input  wire clk,  
    input  wire rst,  
    input  wire in,  
    output reg  detected  
);  
  
    localparam S0  = 2'b00;  
    localparam S1  = 2'b01;  
    localparam S10 = 2'b10;  
  
    reg [1:0] current_state, next_state;  
  
    // Block 1: State register  
    always @(posedge clk or posedge rst) begin  
        // TODO  
    end  
  
    // Block 2: Next state logic  
    always @(*) begin  
        // TODO  
    end  
  
    // Block 3: Output logic (MEALY!)  
    always @(*) begin  
        // TODO: When should detected=1?  
        // Hint: current_state == S10 && in == ???  
    end  
  
endmodule
```
